

# Sheet

## Controlled rectifier

### 1- Single-Phase Half-Wave Controlled Rectifier (Converter)

**Ex 1:**

Single-phase half-wave converter circuit has  $v_s(t) = 120 \sin(377t)$  V and a load resistance  $R = 10 \Omega$ . The delay angle is  $\frac{\pi}{3}$ . Determine:

- (a) The efficiency
- (b) The FF
- (c) The RF
- (d) The TUF
- (e) The PIV of Thyristor

**Ex 2:**

In single-phase half-wave converter with resistive load, draw:

- (a) Power circuit
- (b) Output voltages
- (c) voltage across the Thyristor
- (d) Current through Thyristor
- (e) Load current
- (h) Source current

**Ex 3:**

In single-phase half-wave converter with inductive load, draw:

- (a) Power circuit
- (b) Output voltages
- (c) voltage across the Thyristor
- (d) Current through Thyristor
- (e) Load current
- (h) Source current

**Ex 4:**

In single-phase half-wave converter with resistive load, derive the output voltage using Fourier series