

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

( وَفَوْقَ كُلِّ ذِي عِلْمٍ عَلِيمٌ )

صدق الله العظيم



Tuesday , March, 24 ,2020  
9.00 AM

## Sheet 5

# Rectifier circuits and High voltage Measurements

---

Presenter:

**Hossam H. H. Mousa**

\*[H.Herzallah@eng.svu.edu.eg](mailto:H.Herzallah@eng.svu.edu.eg)


Teaching assistant,  
Department of Electrical Engineering  
South Valley University

## Contents


---

- Rectifier circuits
  1. Half wave rectifier
  2. Center-tab full wave rectifier
  3. Bridge Full wave rectifier
- High voltage Measurements


## Rectifier circuits

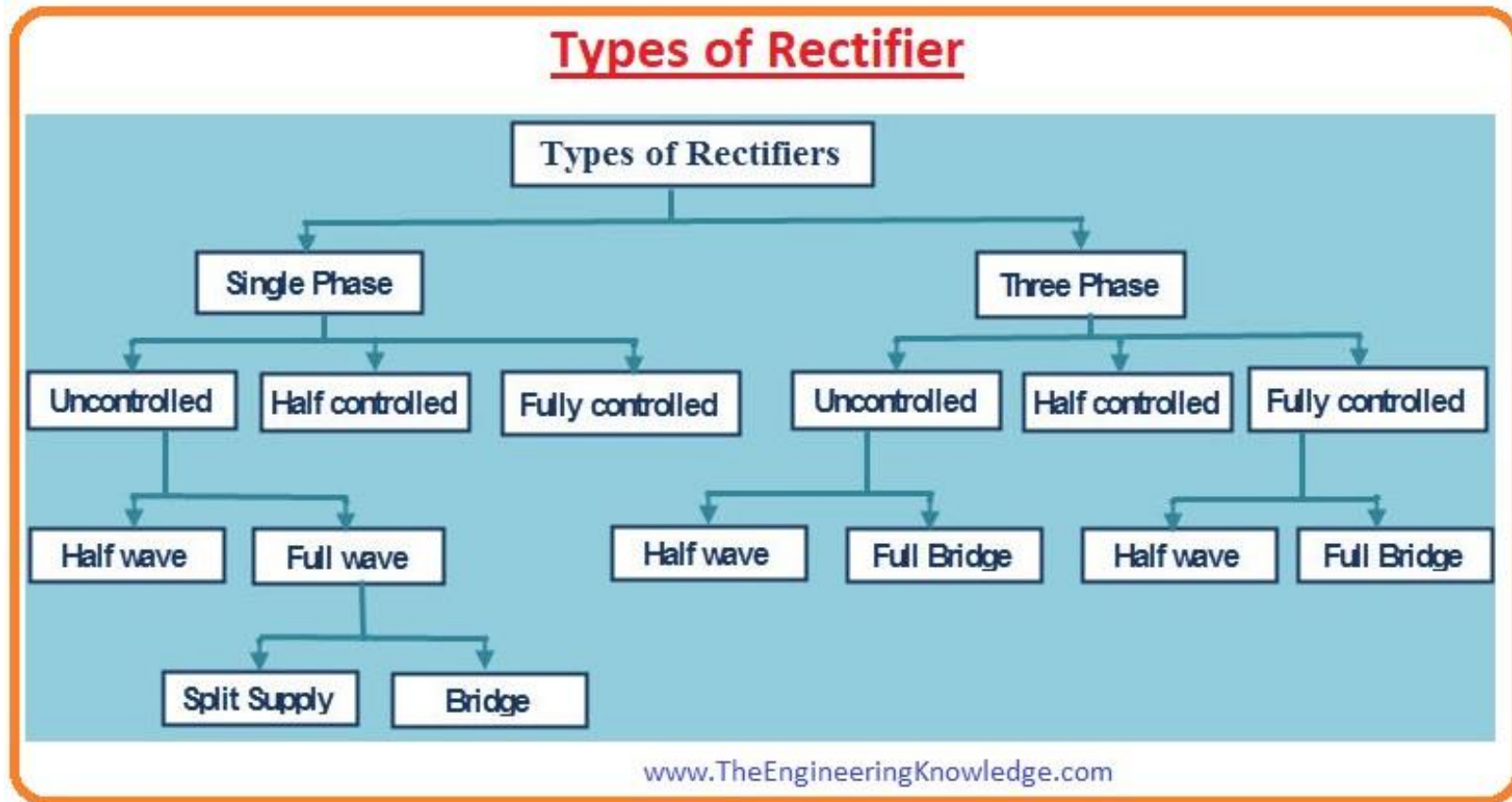



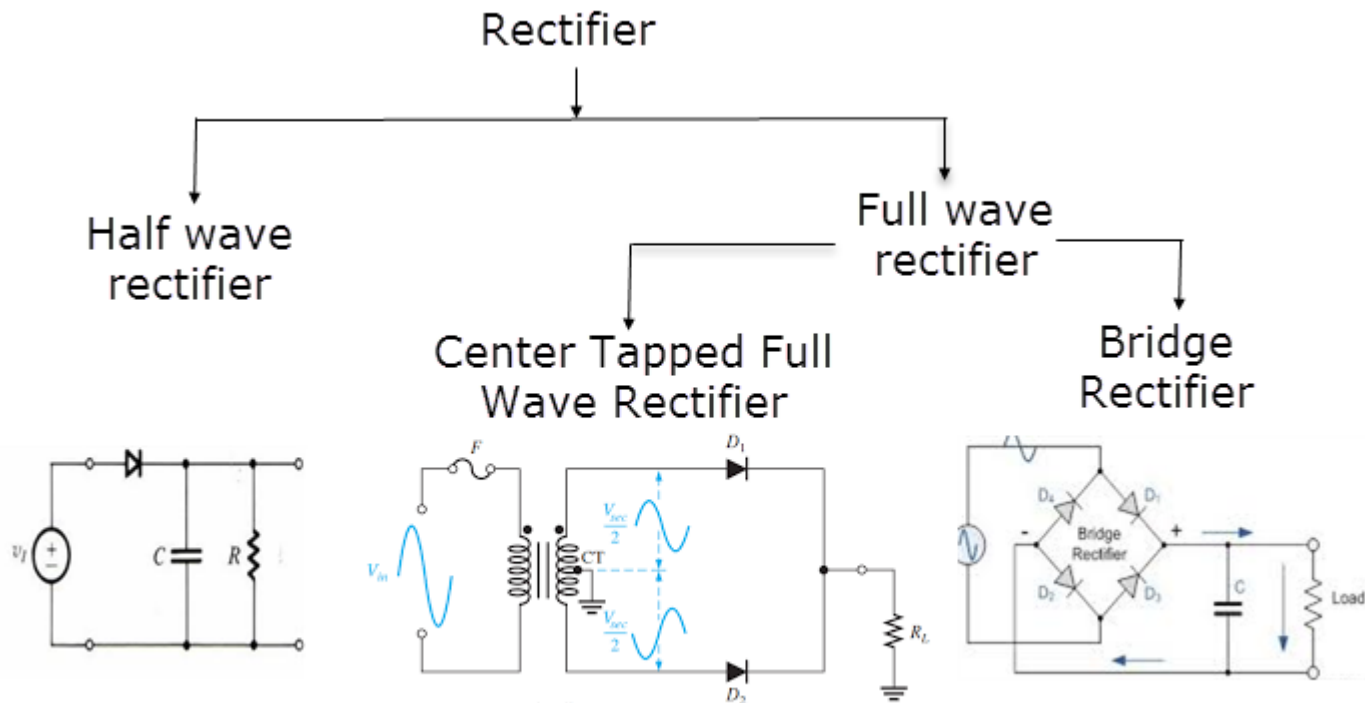
## Single-phase uncontrolled rectifier circuit



## Half wave rectifier

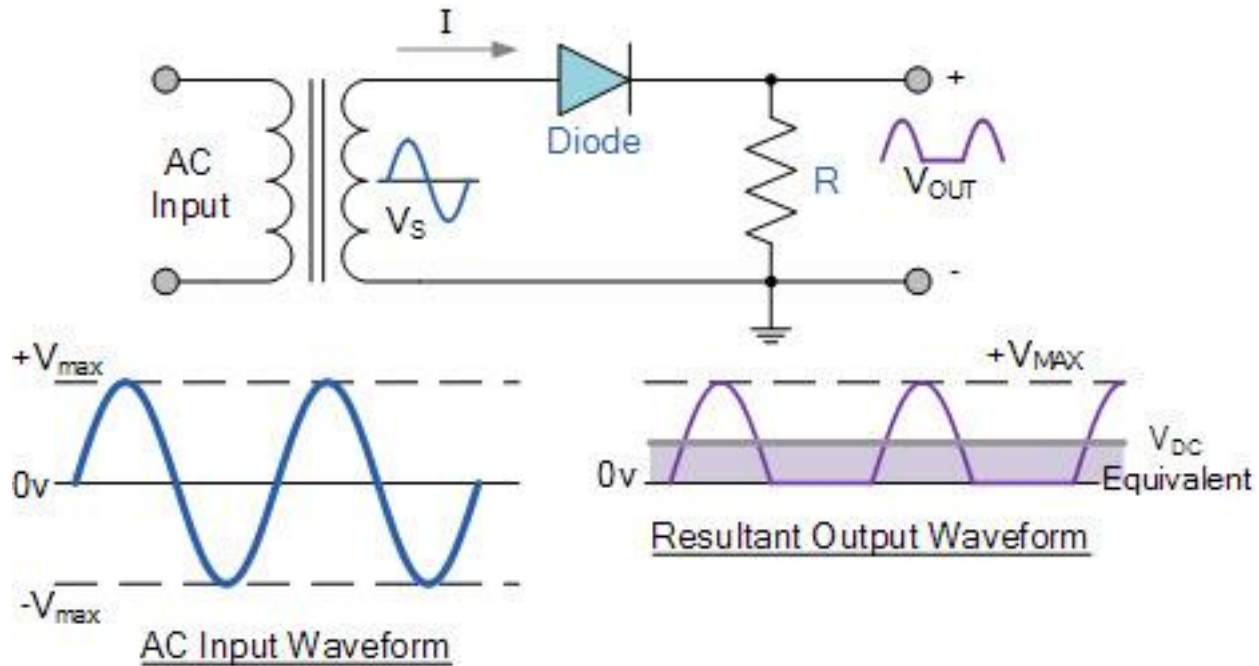


## Center-tab full wave rectifier

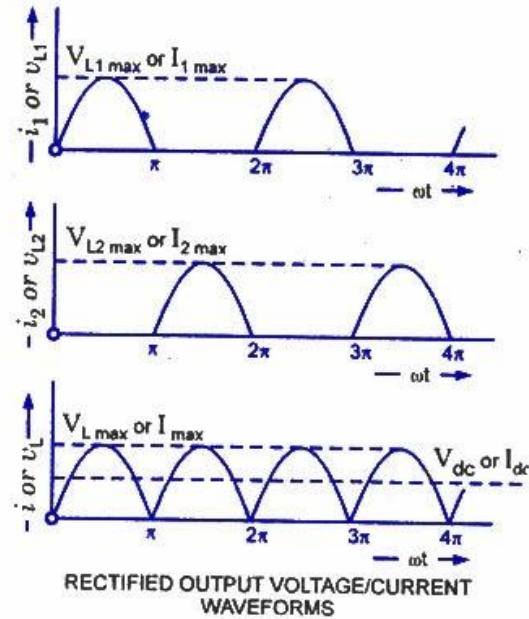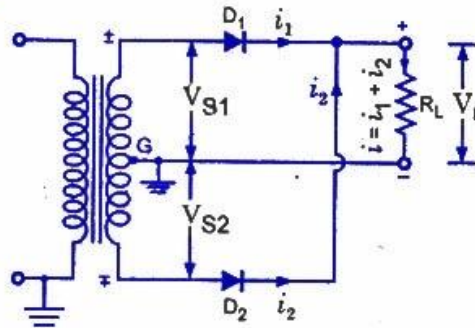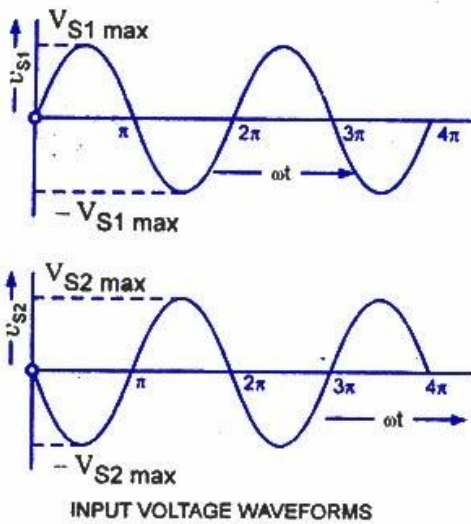


*Centre-Tap Full-Wave Rectifier*

## Bridge Full wave rectifier

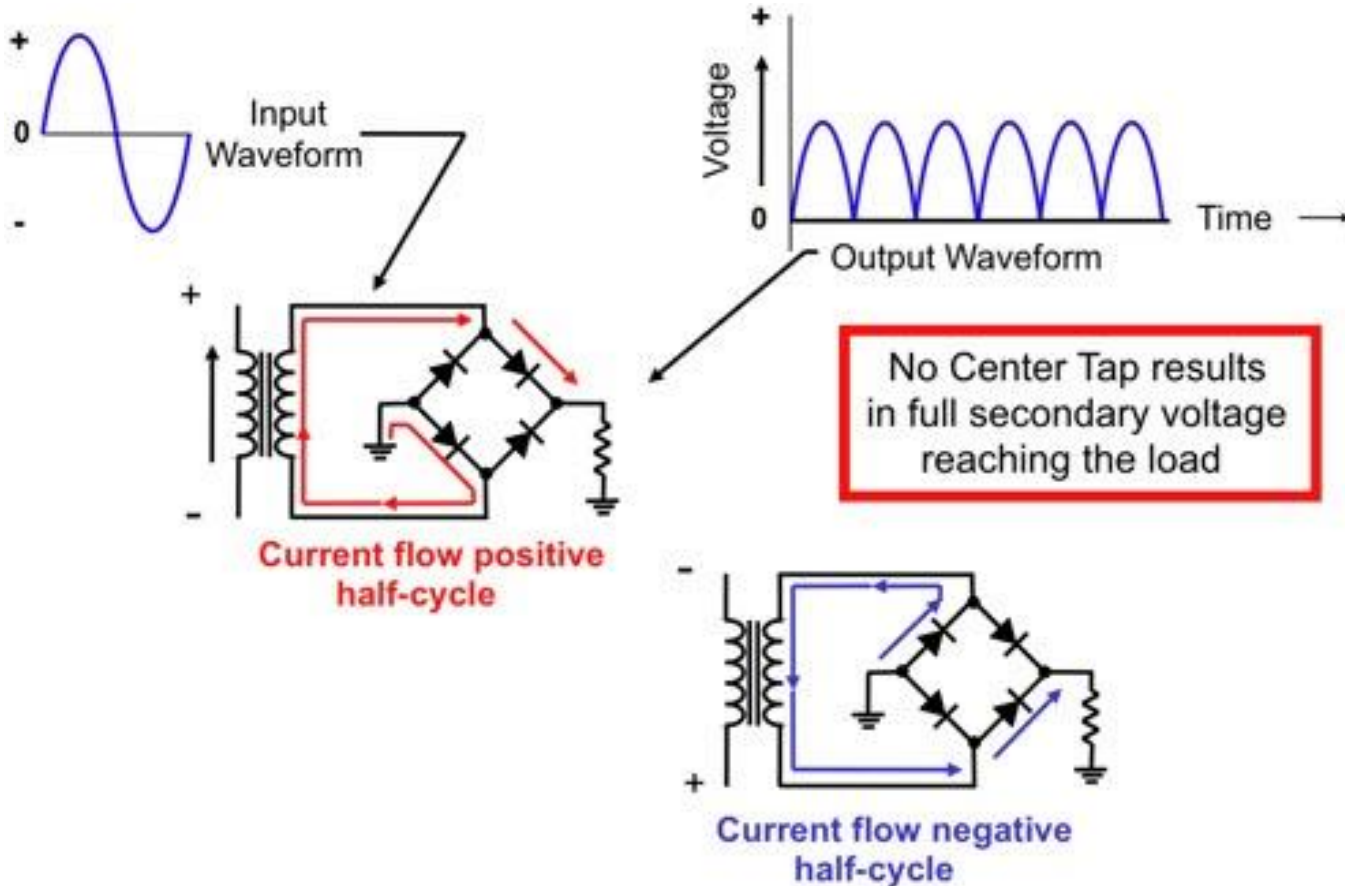



## Smoothing voltage

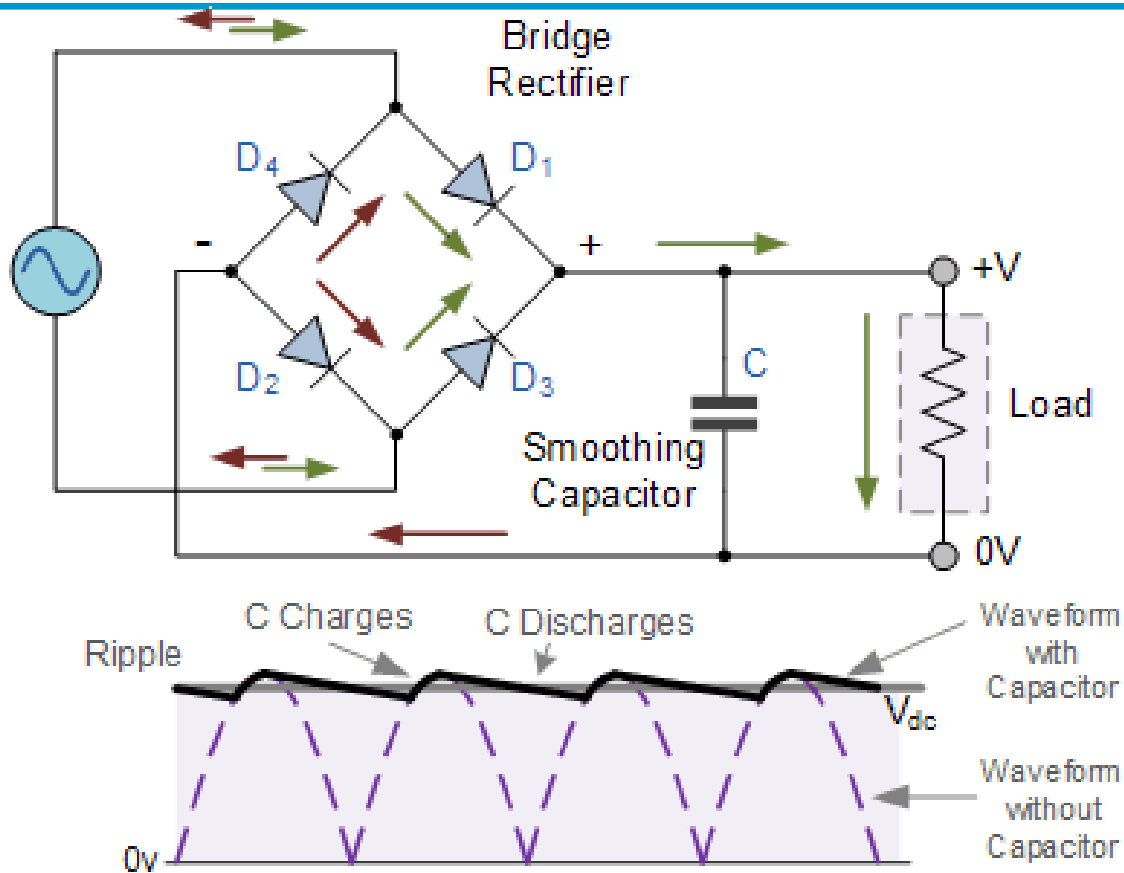


Resultant Output Waveform

## Comparison ???

Rectifier type : Half-wave


Schematic diagram:

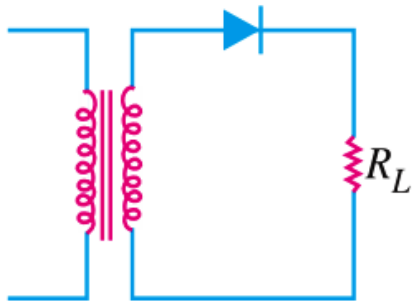


Typical output waveform:



Full-wave Centre-tap

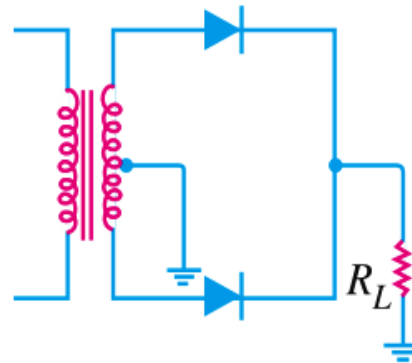

Bridge Rectifier

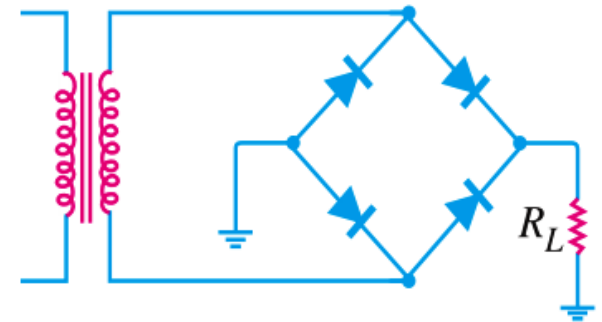



## High voltage ???

- Low Voltage - upto 1000V
- Medium Voltage - 1000V to 35kV
- High Voltage - 35kV to 230 kV
- Extra High Voltage - above 230 kV.

In some situations, the term Ultra High Voltage is used to denote voltages above 800 kV.





## Bar-type current transformer

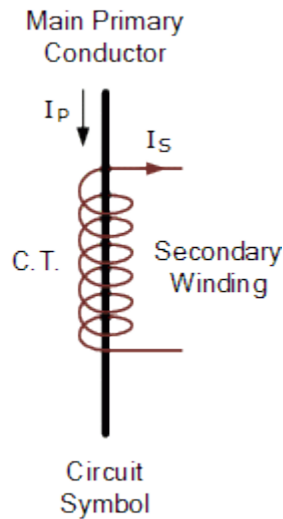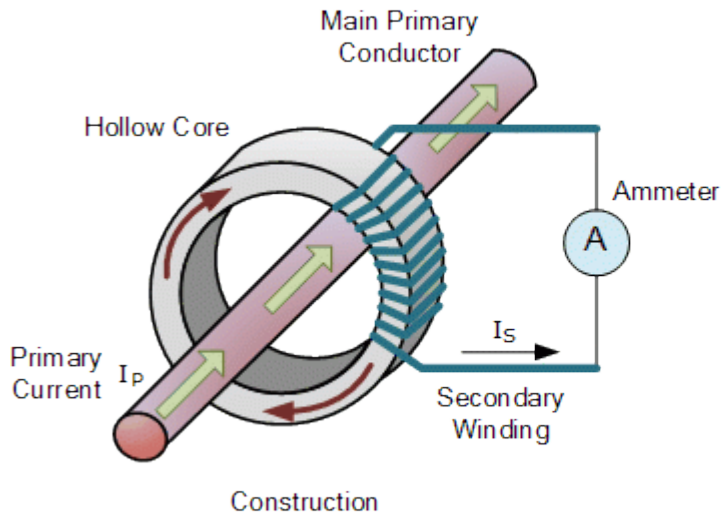

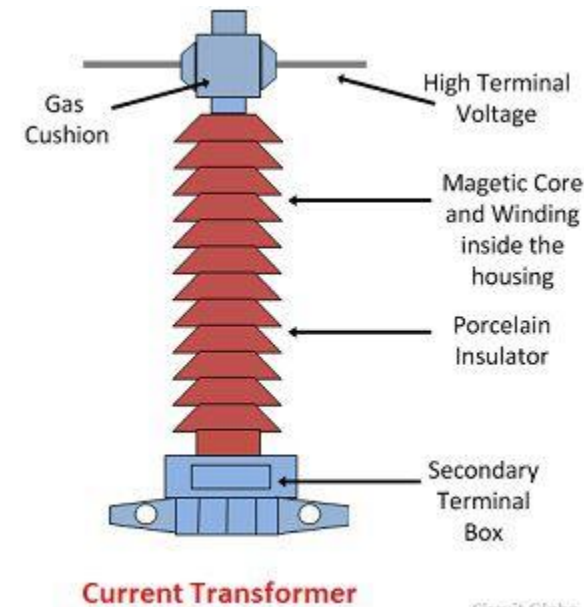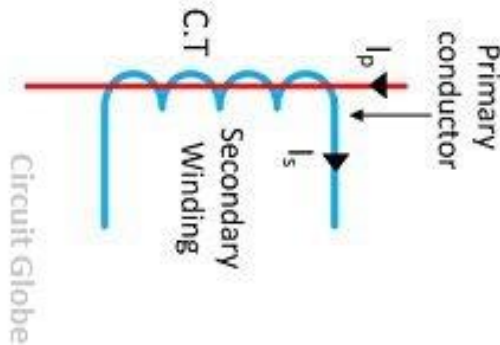
## Series current transformer

- The primary and the secondary windings are insulated from the cores and each other.
- The primary winding is a single turn winding (also called a bar primary) and carries the full load current.
- The secondary winding of the transformers has a large number of turns.




Circuit Globe

# Electrical Drawing

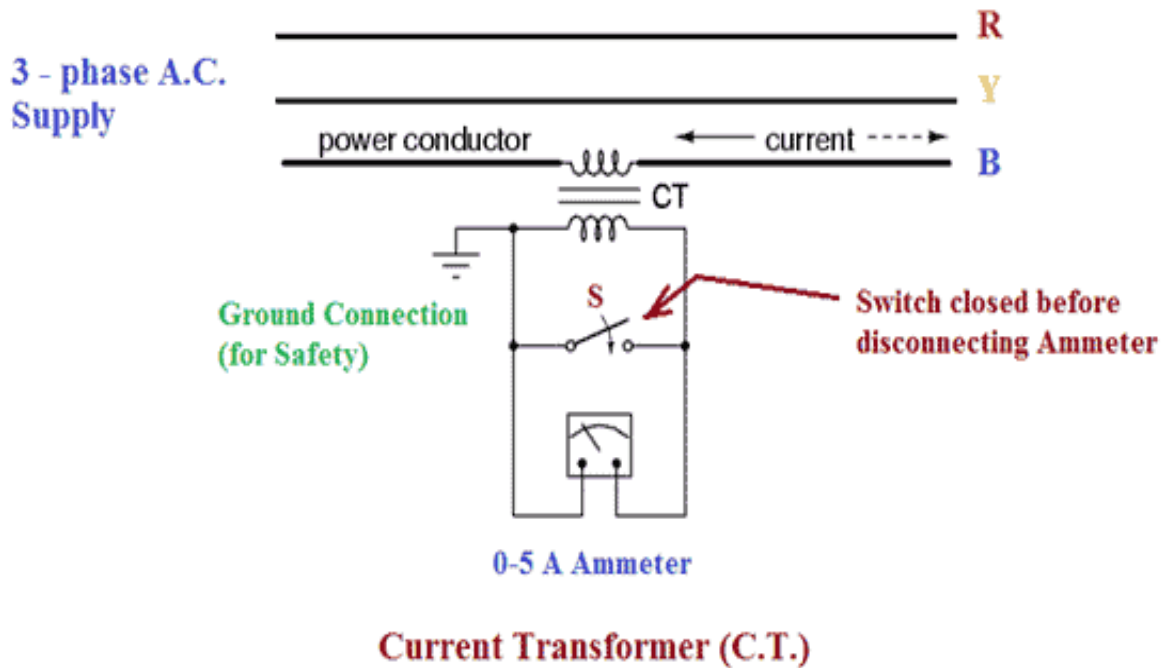


## Protentional transformer

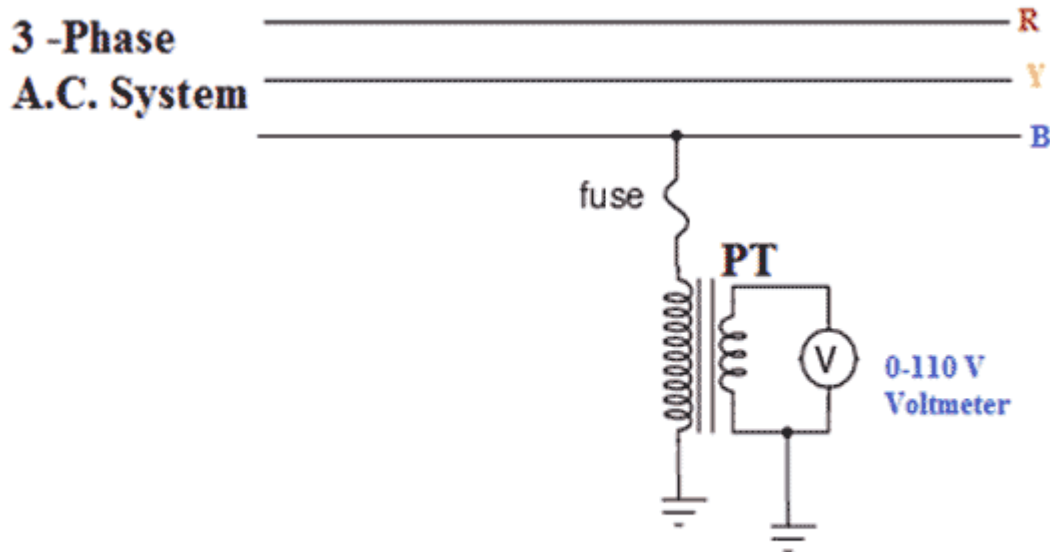


**Potential Transformer (P.T.)**

## General circuit

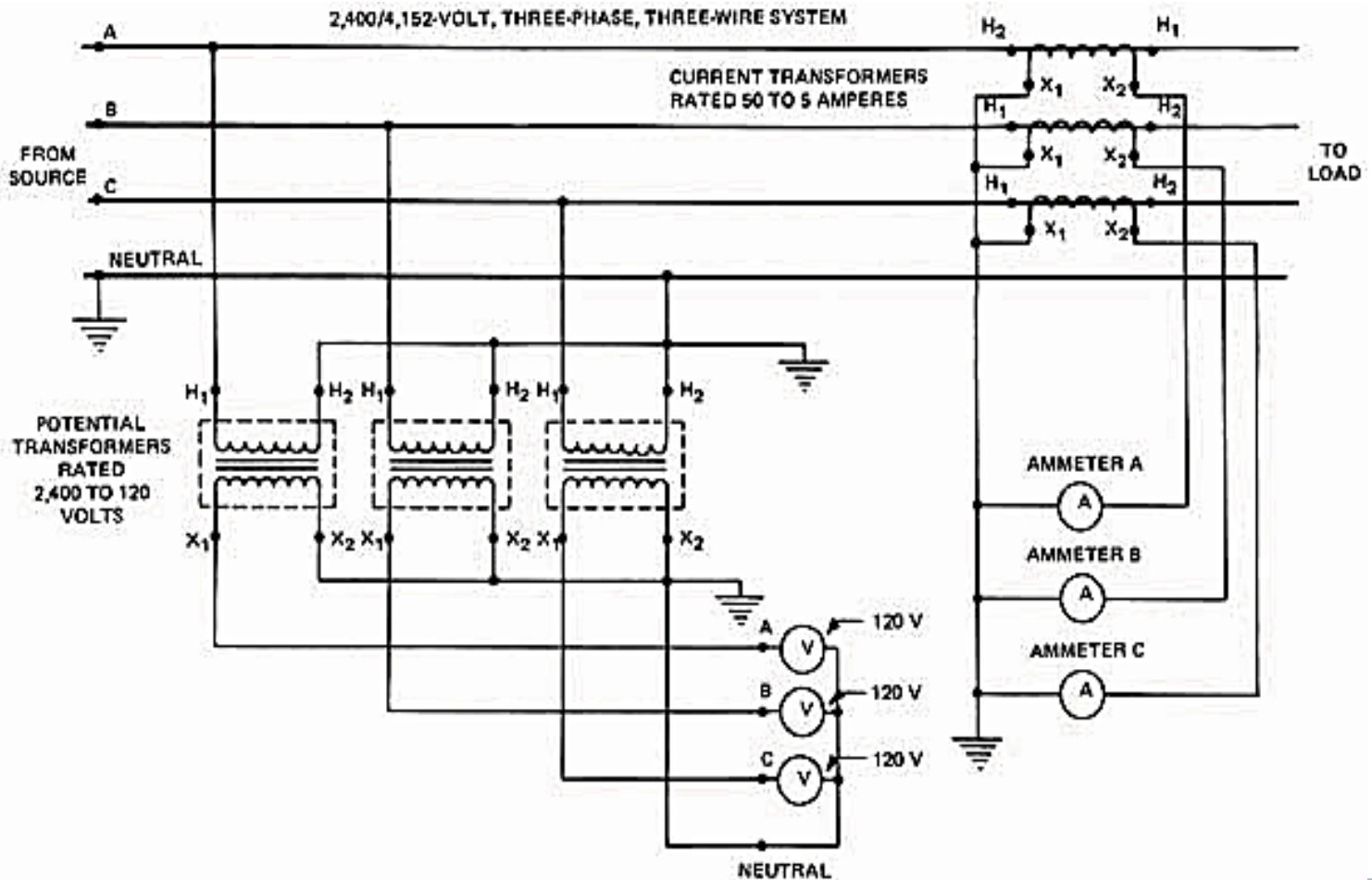




## Drawing 1

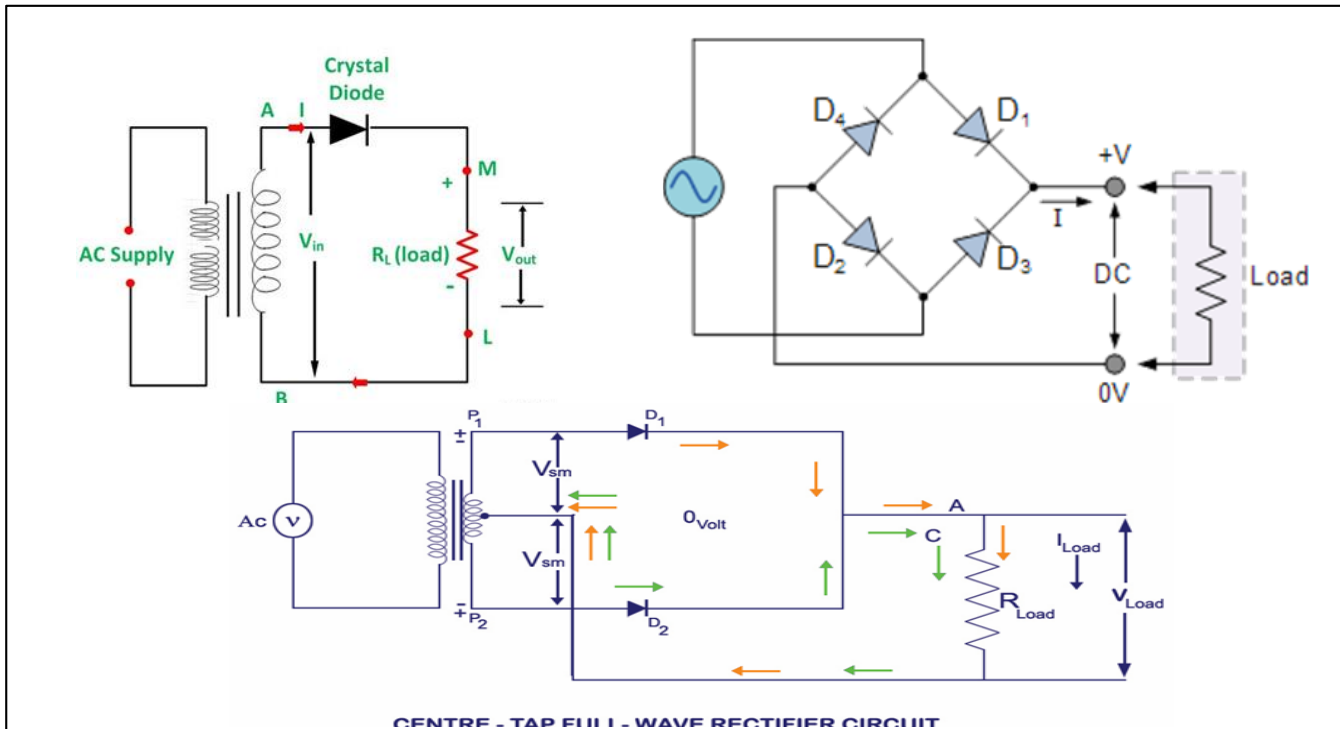

CENTRE - TAP FULL - WAVE RECTIFIER CIRCUIT

South Valley University Faculty of Engineering Department of Electrical Engineering	DRN BY:		MAT	CL. NO	SH NO	Rectifier cir.
	Scale	Dims :mm	WT	B. NO	Date :	



## Drawing 2

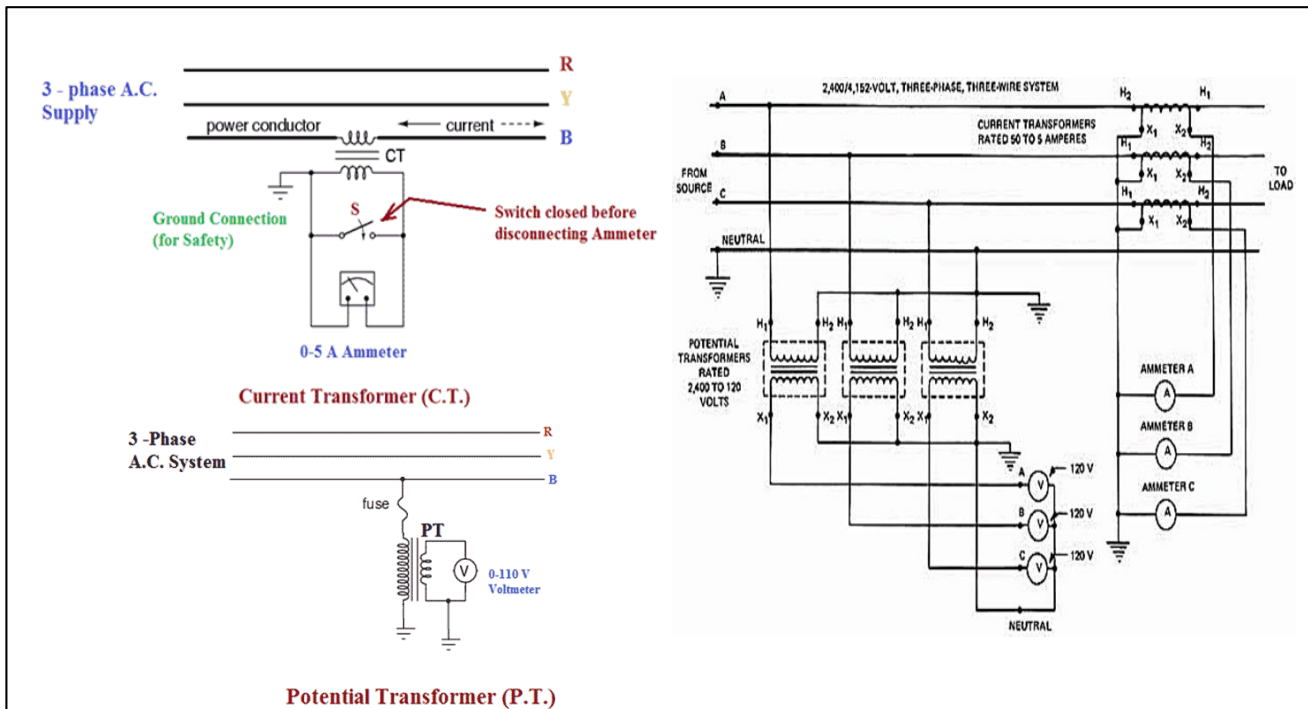

South Valley University Faculty of Engineering Department of Electrical Engineering	DRN BY:		MAT	CL. NO	SH NO	High voltage mea.
	Scale	Dims :mm	WT	B. NO	Date :	
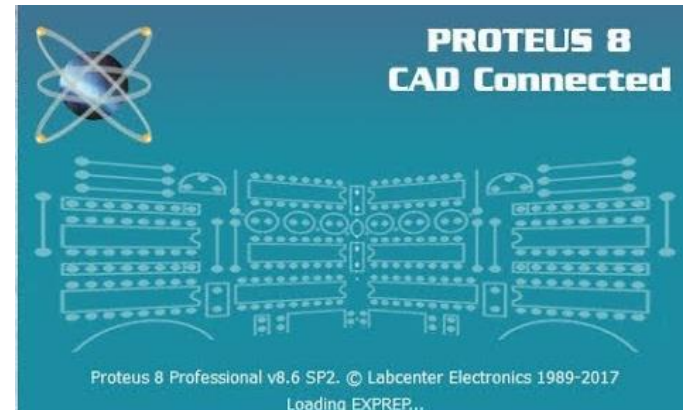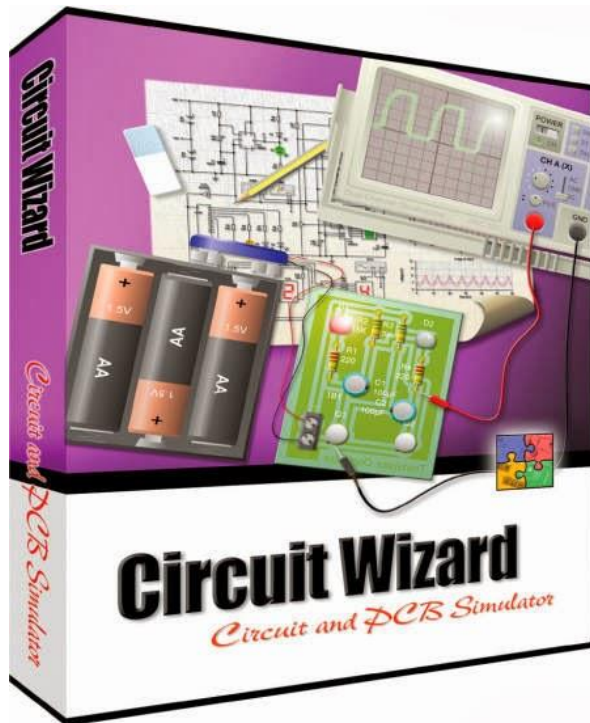
## Task

- Comparison among rectifier circuits and their simulation



# Electrical Drawing

## Feedback

---

**Email: [hossam.herzallah7@gmail.com](mailto:hossam.herzallah7@gmail.com)**

**Email subject: Transformer regulation Feedback**

## Reference

---

- <https://circuitglobe.com/current-transformer-ct.html>
- <https://circuitglobe.com/potential-transformer-pt.html>
- <https://www.electrical4u.com/>

*Thanks*