

Fundamentals of Electric Circuits

CHAPTER 4 CIRCUIT THEOREMS

Dr. Ibrahim Hamdan

Circuit Theorems - Chapter 4

4.4 Source Transformation

Note:- read these parts from Ref (*Fundamentals of Electric Circuits* 'Charles K. Alexander & Matthew N. O. Sadiku')


Source Transformation

4.4 Source Transformation

- An equivalent circuit is one whose v - i characteristics are identical with the original circuit.
- It is the process of replacing a voltage source v_S in series with a resistor R by a current source i_S in parallel with a resistor R , or vice versa.

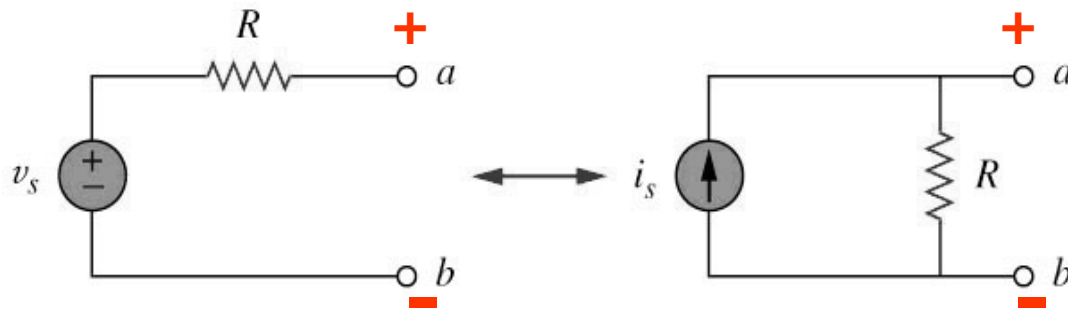4.4 Source Transformation

- The arrow of the current source is directed toward the positive terminal of the voltage source.




Independent source transform

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$

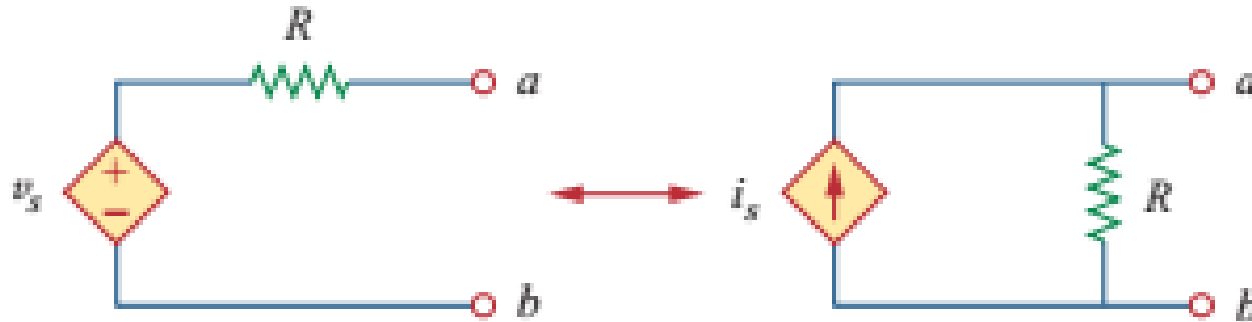4.4 Source Transformation

Source transformation also applies to dependent sources, provided we carefully handle the dependent variable. As shown in Fig. dependent voltage source in series with a resistor can be transformed to a dependent current source in parallel with the resistor or vice versa.



Examples for
source
transformation

Use source transformation to find v_o in the circuit of Fig. 4.17.

Example 4.6

Solution:

We first transform the current and voltage sources to obtain the circuit in Fig. 4.18(a). Combining the 4- Ω and 2- Ω resistors in series and transforming the 12-V voltage source gives us Fig. 4.18(b). We now combine the 3- Ω and 6- Ω resistors in parallel to get 2- Ω . We also combine the 2-A and 4-A current sources to get a 2-A source. Thus, by repeatedly applying source transformations, we obtain the circuit in Fig. 4.18(c).



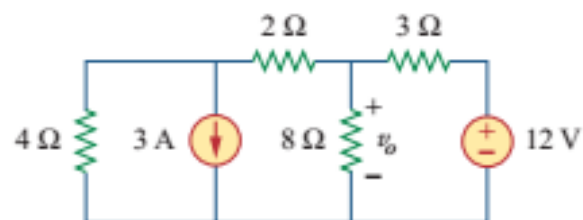



Figure 4.17
For Example 4.6.

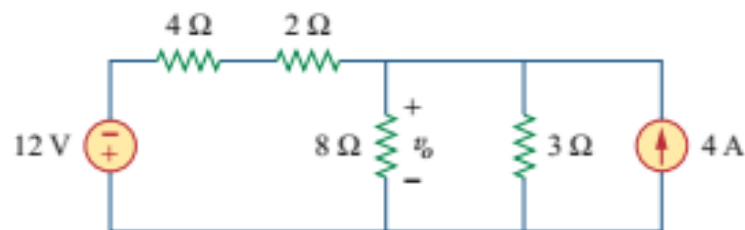

(a)

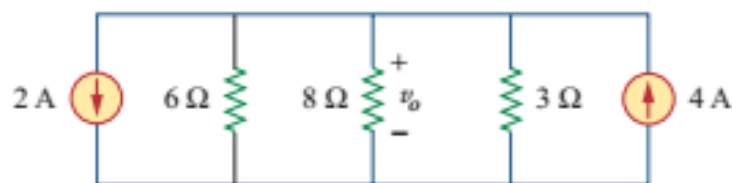

(b)

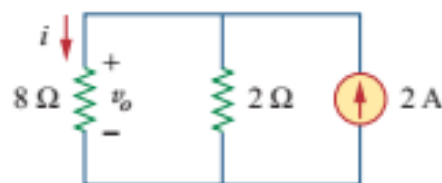

(c)

Figure 4.18
For Example 4.6.

We use current division in Fig. 4.18(c) to get

$$i = \frac{2}{2 + 8}(2) = 0.4 \text{ A}$$

and


$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$

Alternatively, since the 8- Ω and 2- Ω resistors in Fig. 4.18(c) are in parallel, they have the same voltage v_o across them. Hence,


$$v_o = (8 \parallel 2)(2 \text{ A}) = \frac{8 \times 2}{10}(2) = 3.2 \text{ V}$$

Example

- Find i (with source transformation)

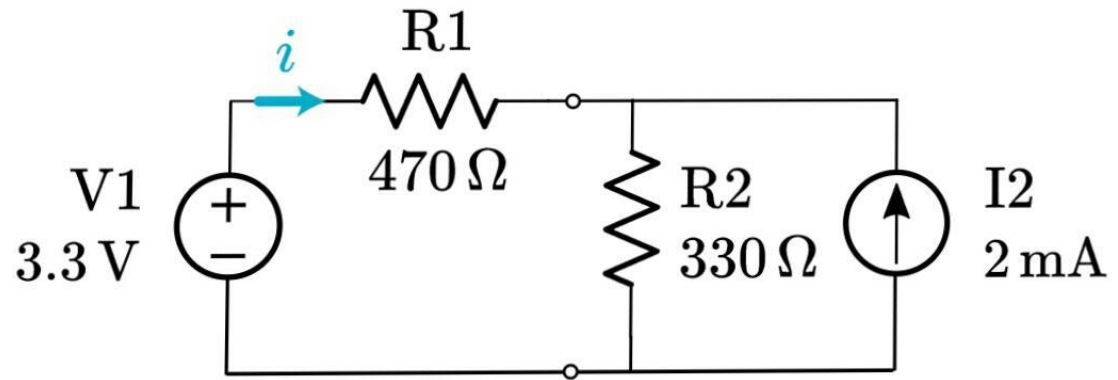

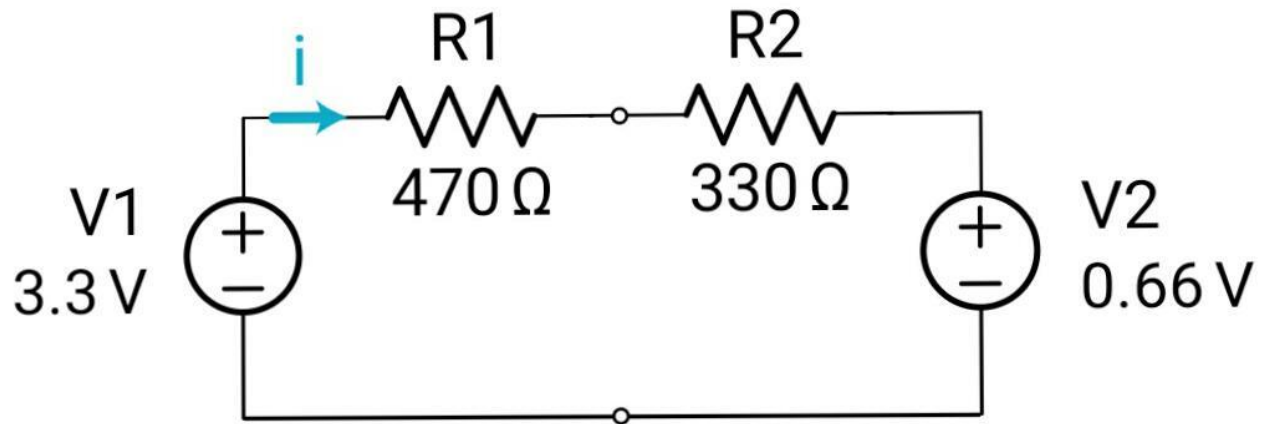- Transform the circuit form to the equivalent form
- **R2** is the same for both .
- **R2 = 330Ω**
- The voltage sources is
- **V2=i2. R2=2mA. 330Ω=0.66V**





- Source transformation gave us two resistors in series. The voltage across the series resistors is **$V_1 - V_2$** .
- Ohm's Law gives us,
- **$i = (V_1 - V_2) \div (R_1 + R_2)$**

- **$i = (3.3 - 0.66) \div (470 + 330)$**


- **$i = 3.3\text{mA}$**

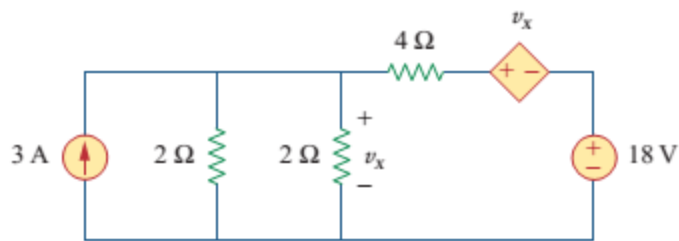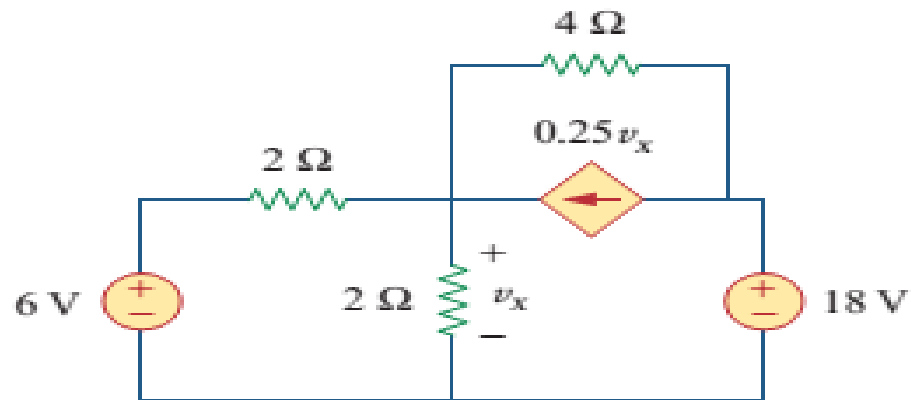Example

Find v_x in Figure using source transformation




(a)

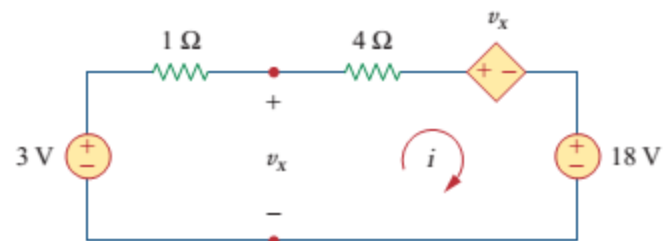


(b)

Solution

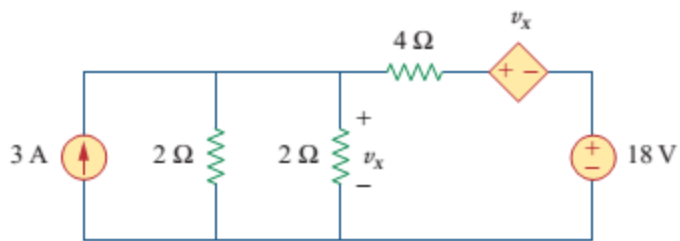

(a)

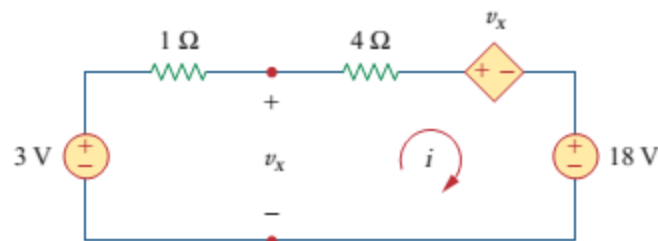

(b)

Applying KVL around the loop in Fig. (b) gives

$$-3 + 5i + v_x + 18 = 0$$

Applying KVL to the loop containing only the 3-V voltage source, the 1-Ω resistor, and v_x yields

$$-3 + 1i + v_x = 0 \quad \Rightarrow \quad v_x = 3 - i$$

$$15 + 5i + 3 - i = 0 \quad \Rightarrow \quad i = -4.5 \text{ A} \quad \text{Thus, } v_x = 3 - i = 7.5 \text{ V.}$$