

# Fundamentals of Electric Circuits

## CHAPTER 4 CIRCUIT THEOREMS

Dr. Ibrahim Hamdan

# Circuit Theorems - Chapter 4

4.3 Superposition

4.4 Source Transformation

Note:- read these parts from Ref (*Fundamentals of Electric Circuits* 'Charles K. Alexander & Matthew N. O. Sadiku')

# Superposition Theorem

## 4.3 Superposition Theorem

The **superposition** principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

## 4.3 Superposition Theorem

### **Steps to Apply Superposition Principle:**

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using any techniques.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.

## 4.3 Superposition Theorem

### Things to keep in mind:


1. When turn off all other independent sources:
  - Independent voltage sources are replaced by 0 V (**short circuit**) and
  - Independent current sources are replaced by 0 A (**open circuit**).
2. Dependent sources **are left** intact because they are controlled by circuit variables.

# Examples for Superposition Theorem


# 4.3 Superposition Theorem
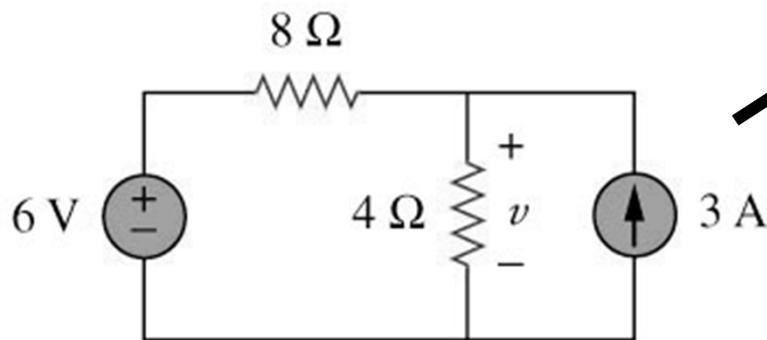
## Example

Use the superposition theorem to find  $v$  in the circuit shown below.




3A is discarded  
by open-circuit

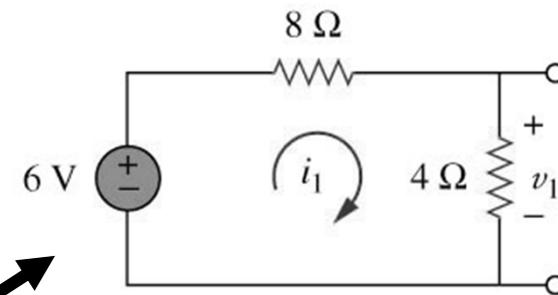

(a)

6V is discarded  
by short-circuit

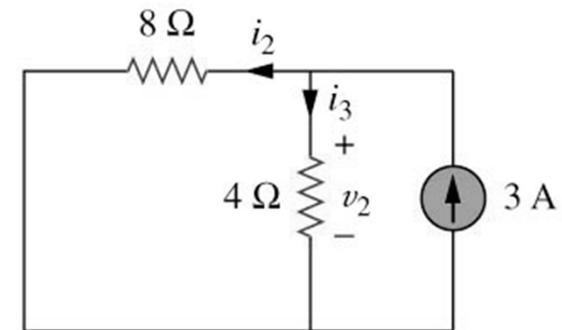

(b)

We consider the effects of 3A and 6V one by one, then add the two effects together for final  $v_o$ .

## Example 4.3

Use the superposition theorem to find  $v$  in the circuit of Fig. 4.6.


### Solution:

Since there are two sources, let



$$v = v_1 + v_2$$

where  $v_1$  and  $v_2$  are the contributions due to the 6-V voltage source and the 3-A current source, respectively. To obtain  $v_1$ , we set the current source to zero, as shown in Fig. 4.7(a). Applying KVL to the loop in Fig. 4.7(a) gives

$$12i_1 - 6 = 0 \quad \Rightarrow \quad i_1 = 0.5 \text{ A}$$

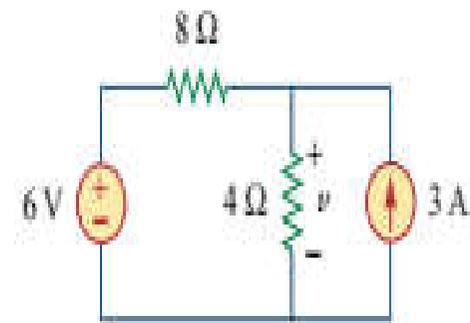

**Figure 4.6**  
For Example 4.3.

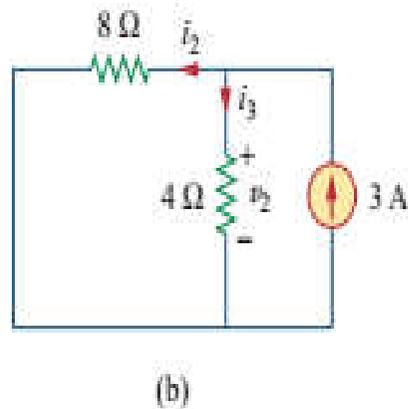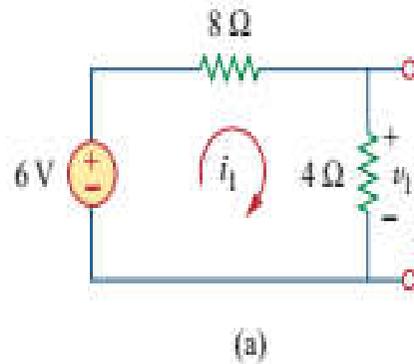

**Figure 4.7**

For Example 4.3: (a) calculating  $v_1$ ,  
 (b) calculating  $v_2$ .

Thus,

$$v_1 = 4i_1 = 2 \text{ V}$$

We may also use voltage division to get  $v_1$  by writing

$$v_1 = \frac{4}{4 + 8}(6) = 2 \text{ V}$$

To get  $v_2$ , we set the voltage source to zero, as in Fig. 4.7(b). Using current division,

$$i_3 = \frac{8}{4 + 8}(3) = 2 \text{ A}$$

Hence,

$$v_2 = 4i_3 = 8 \text{ V}$$


And we find

$$v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$$

## 4.3 Superposition Theorem
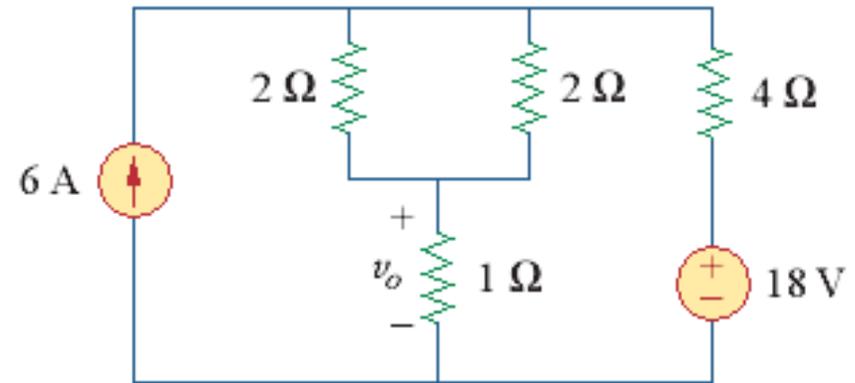
### **Example 1**


Use superposition to find  $v_o$  in the circuit.



### **Solution**

Let  $v_o = v_1 + v_2$ , where  $v_1$  and  $v_2$  are due to 6-A and 20-V sources respectively.

We find  $v_1$  using the circuit below.

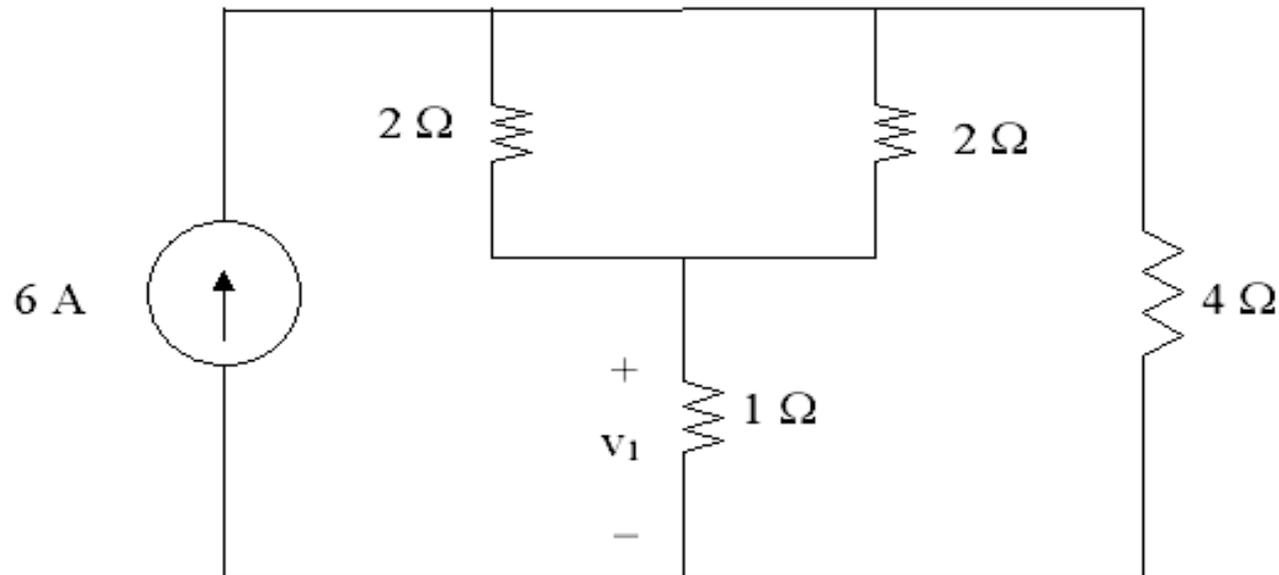


## 4.3 Superposition Theorem

$$2//2 = 1 \Omega, \quad v_1 = 1 \times \frac{4}{4+2}(6A) = 4 \text{ V}$$

We find  $v_2$  using the circuit below.
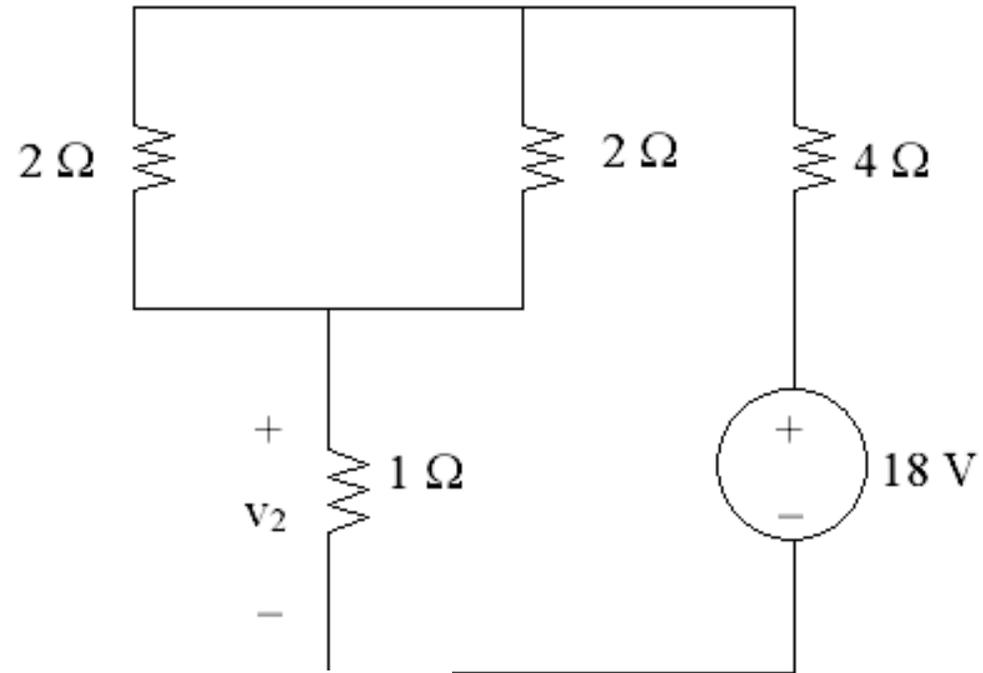
$$v_2 = \frac{1}{1+1+4}(18) = 3 \text{ V}$$



$$v_o = v_1 + v_2 = 4 + 3 = \underline{\underline{7 \text{ V}}}$$




# Source Transformation

## 4.4 Source Transformation

- An equivalent circuit is one whose  $v$ - $i$  characteristics are identical with the original circuit.
- It is the process of replacing a voltage source  $v_S$  in series with a resistor  $R$  by a current source  $i_S$  in parallel with a resistor  $R$ , or vice versa.
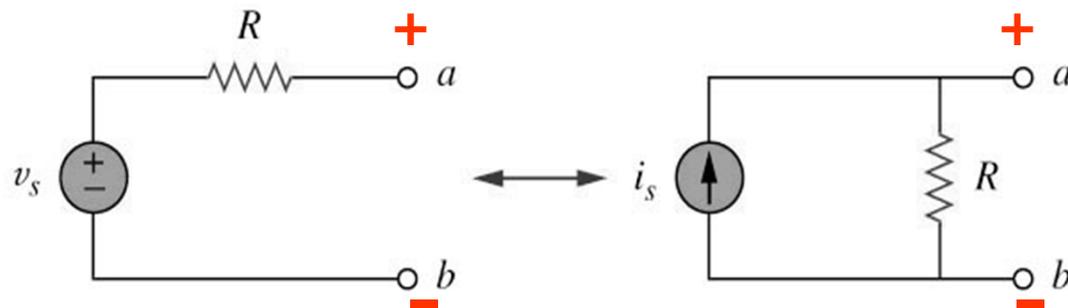
## 4.4 Source Transformation

- The arrow of the current source is directed toward the positive terminal of the voltage source.




Independent source transform

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$
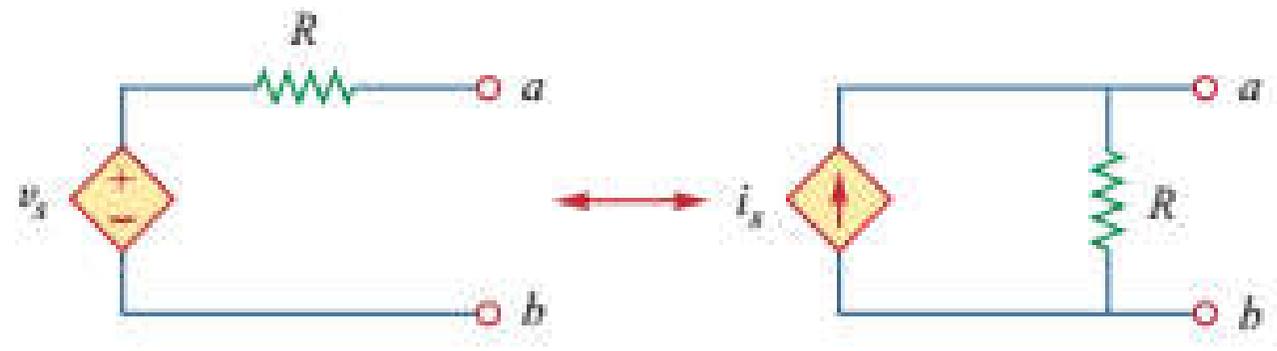
# 4.4 Source Transformation

Source transformation also applies to dependent sources, provided we carefully handle the dependent variable. As shown in Fig. dependent voltage source in series with a resistor can be transformed to a dependent current source in parallel with the resistor or vice versa.




# Examples for source transformation

Use source transformation to find  $v_o$  in the circuit of Fig. 4.17.


### Example 4.6

#### Solution:


We first transform the current and voltage sources to obtain the circuit in Fig. 4.18(a). Combining the  $4\text{-}\Omega$  and  $2\text{-}\Omega$  resistors in series and transforming the  $12\text{-V}$  voltage source gives us Fig. 4.18(b). We now combine the  $3\text{-}\Omega$  and  $6\text{-}\Omega$  resistors in parallel to get  $2\text{-}\Omega$ . We also combine the  $2\text{-A}$  and  $4\text{-A}$  current sources to get a  $2\text{-A}$  source. Thus, by repeatedly applying source transformations, we obtain the circuit in Fig. 4.18(c).

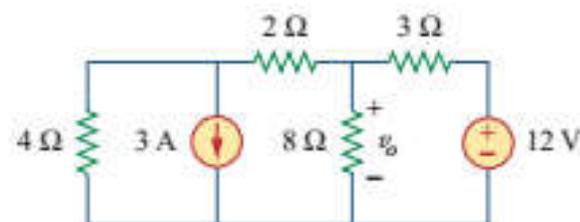


**Figure 4.17**  
For Example 4.6.

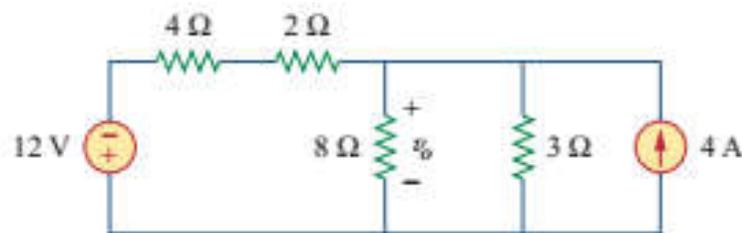

(a)

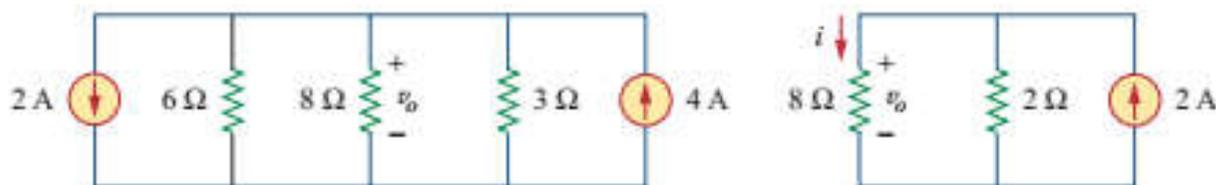

(b)

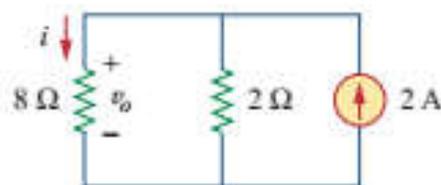

(c)

**Figure 4.18**  
For Example 4.6.

We use current division in Fig. 4.18(c) to get

$$i = \frac{2}{2 + 8}(2) = 0.4 \text{ A}$$

and


$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$

Alternatively, since the 8- $\Omega$  and 2- $\Omega$  resistors in Fig. 4.18(c) are in parallel, they have the same voltage  $v_o$  across them. Hence,


$$v_o = (8 \parallel 2)(2 \text{ A}) = \frac{8 \times 2}{10}(2) = 3.2 \text{ V}$$
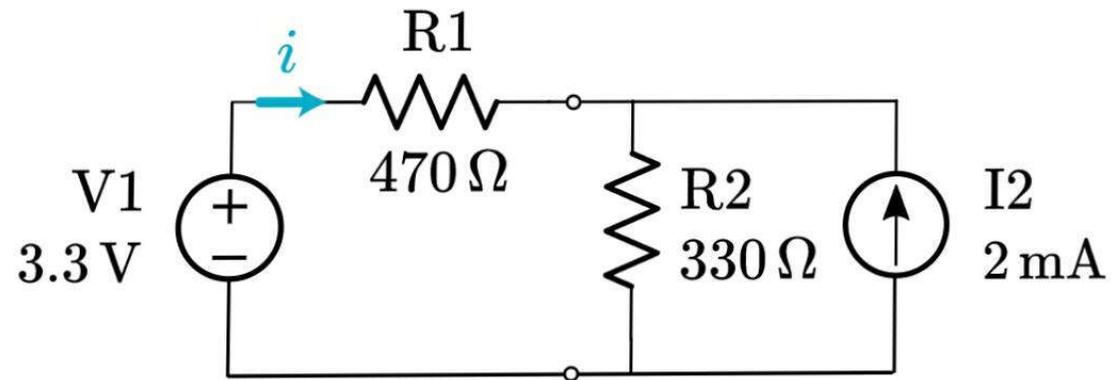
# Example

- Find  $i$  (with source transformation)



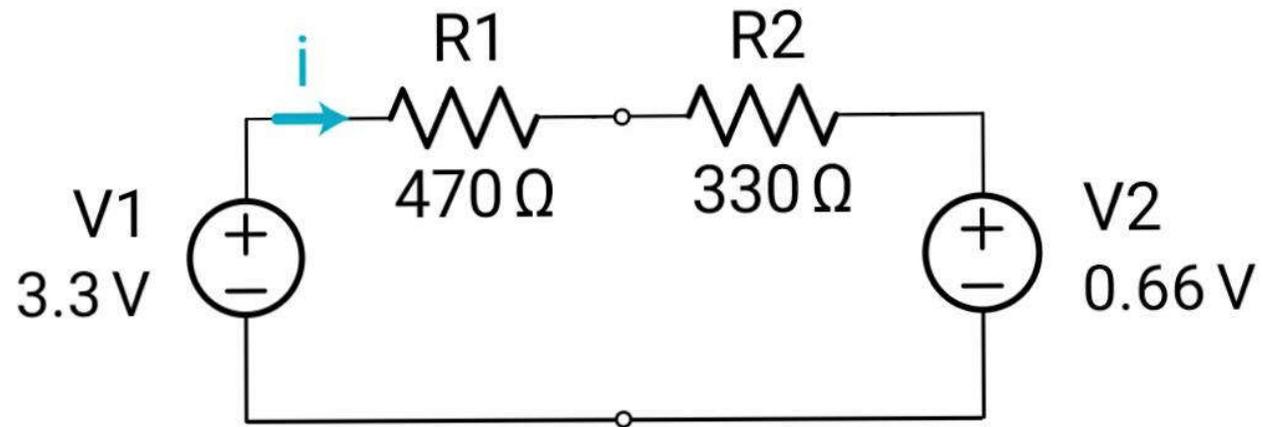- Transform the circuit form to the equivalent form
- **R2** is the same for both .
- **R2 = 330Ω**
- The voltage sources is
- **V2=i2    R2=2mA    330Ω=0.66V**



- Source transformation gave us two resistors in series. The voltage across the series resistors is  **$V_1$   $V_2$**  .
- Ohm's Law gives us,
- **$i = (V_1 + V_2) \div (R_1 + R_2)$**
  
- **$i = (3.3 + 0.66) \div (470 + 330)$**
  
- **$i = 3.3\text{mA}$**